

Combinational building Blocks.

DATE / /
PAGE NO.


Unit - II

Combinational circuit is a circuit in which we combine the different gates in circuit.
eg:- Encoder, Decoder, multiplexer & demultiplexer.

Characteristics of combinational circuit :-

- (1) The output of combinational circuit at any instant of time, depends only on the levels present at input terminals.
- (2) The combinational circuit do not use any memory. The previous state of input does not have any affect on the present state of any the circuit.
- (3) A combinational circuit can have an 'n' number of inputs & m number of outputs.

Block diagram:-

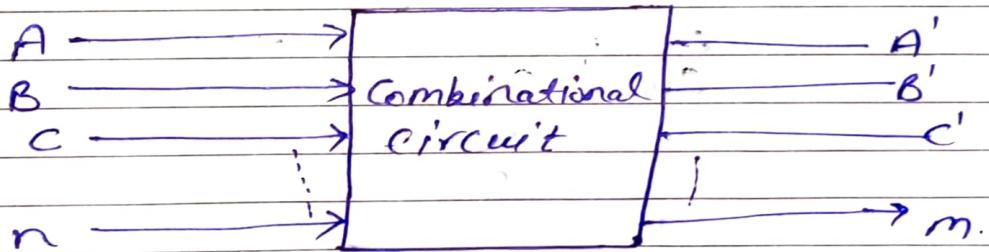


Designing of Combinational circuit

- (1) find the number of inputs & outputs
- (2) write the truth table.
- (3) write the logical Expression.
- (4) Minimize the logical Expression.
- (5) Hardware implementation.

(i)

Half Adder :- The half adder is a basic building block having two inputs & two outputs. The adder is used to perform OR operation of two single bit binary numbers. The Carry & Sum are two output states of the half adder.

Block diagram:-

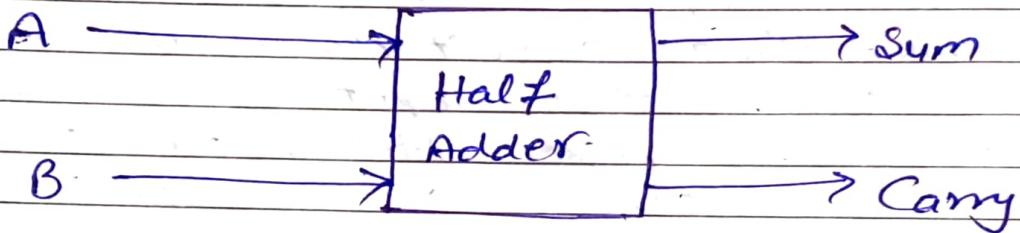

Truth Table

Inputs		Outputs		
A	B	Sum	Carry	→ MSB
0	0	0	0	
0	1	1	0	
1	0	1	0	
1	1	0	1	

In the above table,

- (1) 'A' and 'B' are the input states, and 'sum' & 'Carry' are the output states.
- (2) The 'Carry' output is 0 in case where both the inputs are not 1.
- (3) The least significant bit of the sum is defined by the 'Sum' bit.

The SOP form of the sum & carry are as follows:-

$$\text{Sum} = \bar{x}'y + xy' \quad \text{min term (SOP) } \bar{x}=0, \bar{y}=1$$

$$\text{Carry} = \bar{xy}$$

Construction of half Adder circuit :-


The half adder is designed with the help of the following two logic gates:-

(1) 2-input AND gate.


(2) 2-input Exclusive-OR gate or En-OR gate.

$$\text{Sum} = \bar{x}'y + xy' \quad \text{OR} \quad \text{Sum} = \bar{x} \oplus y$$

$$\text{Carry} = \bar{xy}$$

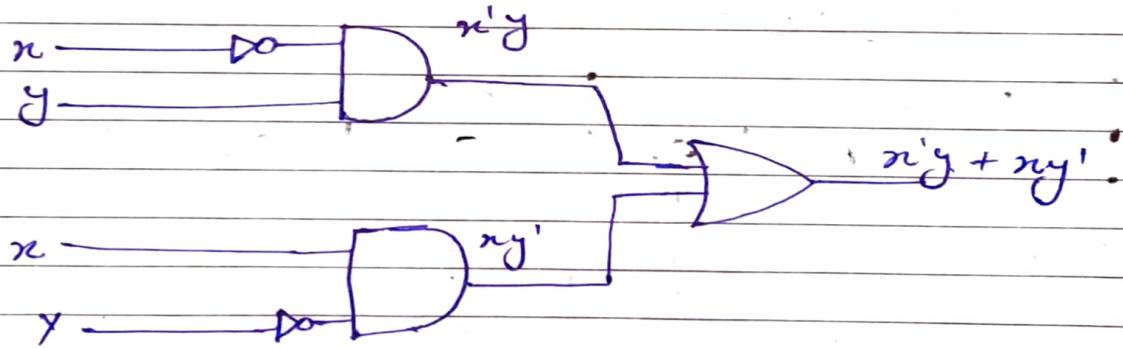


OR

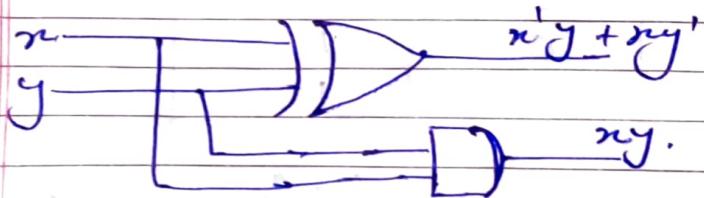

Half-Adder circuit

Full Adder :- The half adder is used to add only two numbers. To overcome this problem, the full adder was developed. The full adder is used to add three 1 bit binary numbers A, B & carry C. The full adder has three input states & two output States i.e; Sum & Carry.

Block diagram :-

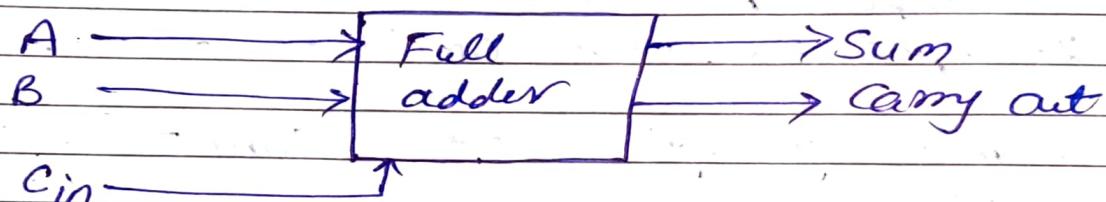

Truth Table

Inputs			Outputs	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(1) 'A' & 'B' are the input variables. These variables represent the two significant bits which are going to be added.

- (2) 'Cin' is the third input which represents the carry from the previous lower significant position, the carry bit is latched.
- (3) The sum & carry are the output variables that define the output values.
- (4) The eight rows under the input variable designate all possible combinations of 0 & 1 that can occur in these variables.

The SOP form can be obtained with the help of K-map as:-

	$x'y'z$	$x'yz$	$xy'z'$	xyz
$x'y'z$	00	01	11	10
$x'yz$	0	1	1	1
$xy'z'$	1	1	1	1
xyz	1	1	1	1

$$\text{Sum} = x'y'z + x'yz + xy'z' + xyz$$

	$x'y'z$	$x'yz$	$xy'z'$	xyz
$x'y'z$	00	01	11	10
$x'yz$	0	1	1	1
$xy'z'$	1	1	1	1
xyz	1	1	1	1

$$\text{Carry} = xy + xz + yz$$

Construction of full adder using half adder:-


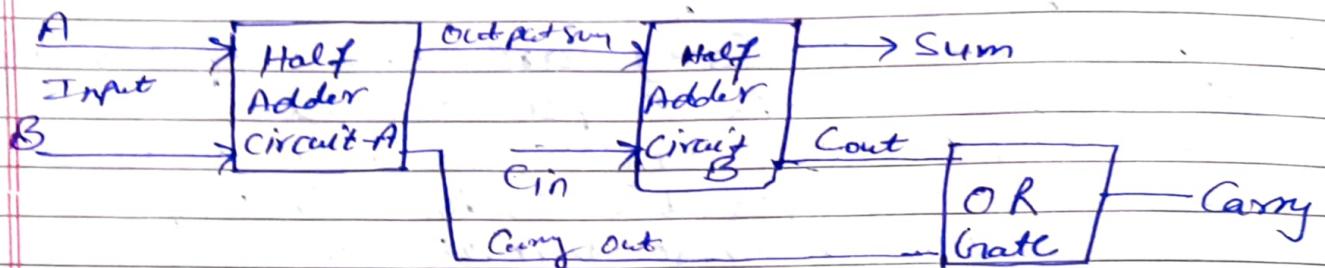


Fig:- Block diagram of full adder

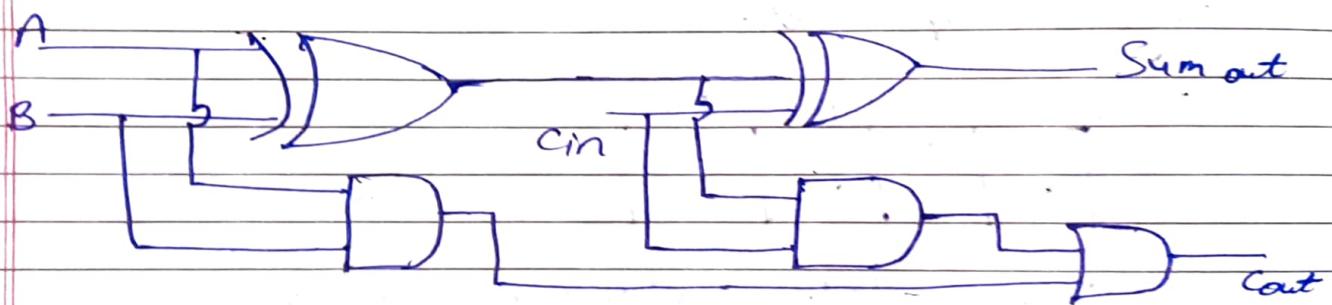

full adder circuit

Sum :- * Perform the XOR operation of input A & B.

(*) Perform the XOR operation of the outcome with Cin. So, the sum is $(A \oplus B) \oplus Cin$ which is also represented as $(A \oplus B) + Cin$.

Carry:- * perform the 'AND' operation of input A & B.

(*) Perform the 'XOR' operation of input A & B.

(*) Perform the 'OR' operations of both the OP that come from the previous two steps. So the 'Carry' can be represented as:- $A \cdot B + (A \oplus B)$

Subtractor :- A subtractor is a combinational logic circuit that can perform the subtraction of two numbers (binary) & produce the difference between them. It is a combinational circuit that means its output depends on its present inputs only. There are two types of subtractors.

- (1) Half Subtractor
- (2) Full Subtractor

(1) Half Subtractor :- It is a combinational circuit which is used to perform subtraction of two bits. It has two inputs & two outputs. Output is known as Difference & Borrow. The logic symbol & truth table are shown below:-



fig:- Logic symbol. of Half Subtractor


Truth Table :-

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean Expression

$$\text{Diff} = A \oplus B$$


$$\text{Borrow} = A'B$$

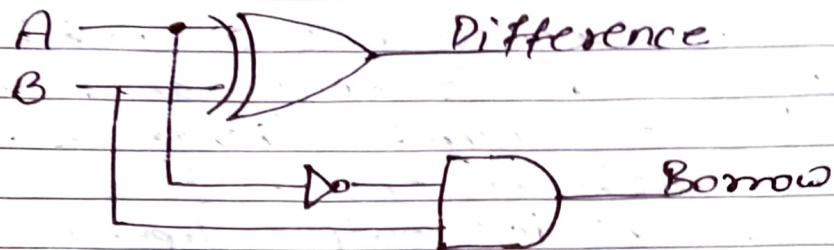

* Circuit diagram *

② full subtractor :- It is a combinational circuit that performs subtraction involving three bits, namely A, B & Bin (Borrow-in). It accepts three inputs A, B & Bin & it produces two outputs: D (difference) & Bout (Borrow out).

Logic Symbol :-

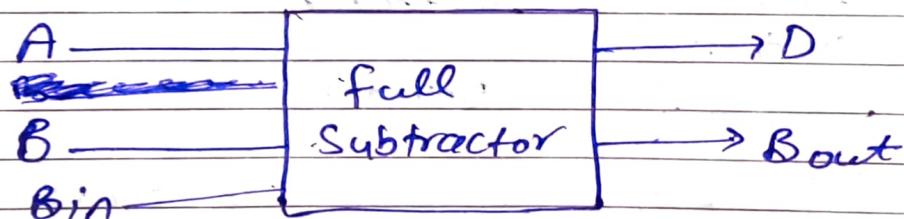


A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Boolean Expression :-

$$D = A \oplus B \oplus B_{in}$$

$$B_{out} = A'B_{in} + A'B + BB_{in}$$

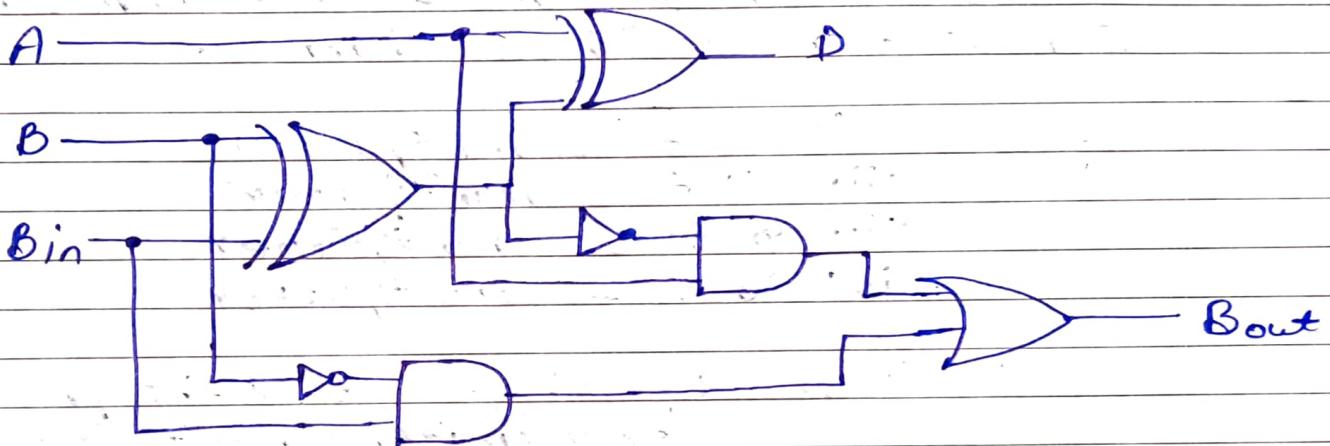


circuit diagram of full subtractor

Encoder in Digital Logic :- An encoder is a digital circuit that converts a set of binary inputs in to a unique binary code. The binary code represents the position of the input & is used to identify the specific input that is active. Encoders are commonly used in digital system to convert a parallel set of inputs in to a serial code.

The combinational circuits that change the binary information into N output lines are known as Encoders. The binary information is passed in the form of 2^N input lines. The output lines define the N -bit code for the binary information.

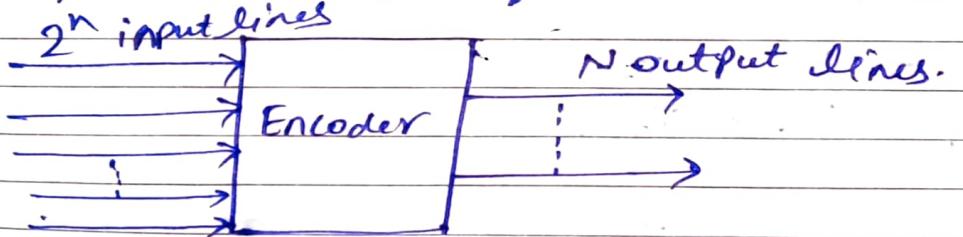
Encoder performs the reverse operation of the decoder. At a time, only one input line is activated for simplicity. The produced N -bit output code is equivalent to the binary information.



There are various types of encoders which are as follows:-

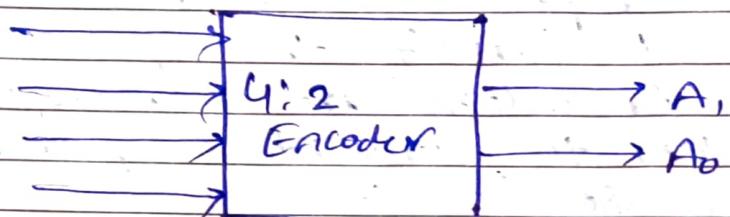- (1) 4 to 2 line Encoder :- In 4 to 2 line encoder, there are total of four inputs i.e., Y_0, Y_1, Y_2, Y_3 & two outputs i.e., A_0, A_1 .

In 4-input lines, one input line is set to true at a time to get the respective binary code.




INPUTS				Outputs	
y_0	y_1	y_2	y_3	A_1	A_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Boolean Expression:-

$$\begin{aligned} A_1 &= Y_2 + Y_3 \\ A_0 &= Y_1 + Y_3 \end{aligned}$$


Logic Diagram

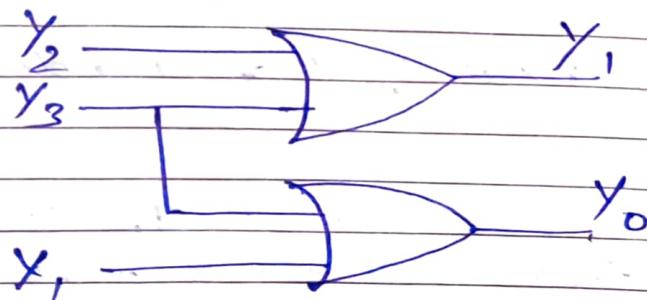

(*) 8 : 3 Encoder (Octal to binary Encoder) :-

8 → Input line

3 → Output line.

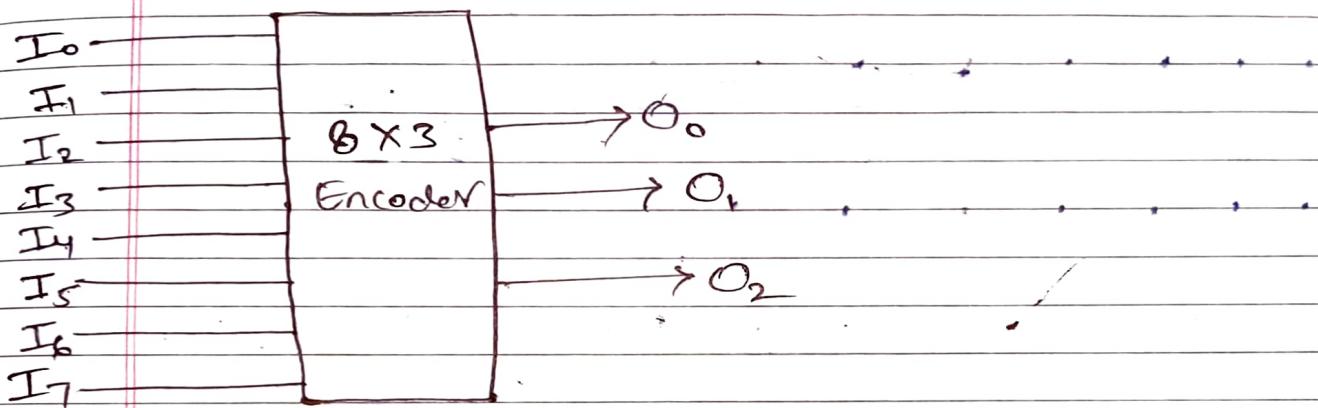


	Input								Output		
	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	O_2	O_1	O_0
0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	1
2	0	0	1	0	0	0	0	0	0	1	0
3	0	0	0	1	0	0	0	0	0	1	1
4	0	0	0	0	1	0	0	0	1	0	0
5	0	0	0	0	0	1	0	0	1	0	1
6	0	0	0	0	0	0	1	0	1	1	0
7	0	0	0	0	0	0	0	1	1	1	1

$$O_2 \rightarrow I_4 + I_5 + I_6 + I_7$$

$$O_1 \rightarrow I_2 + I_3 + I_6 + I_7$$

$$O_0 \rightarrow I_1 + I_3 + I_5 + I_7$$

Logic diagram

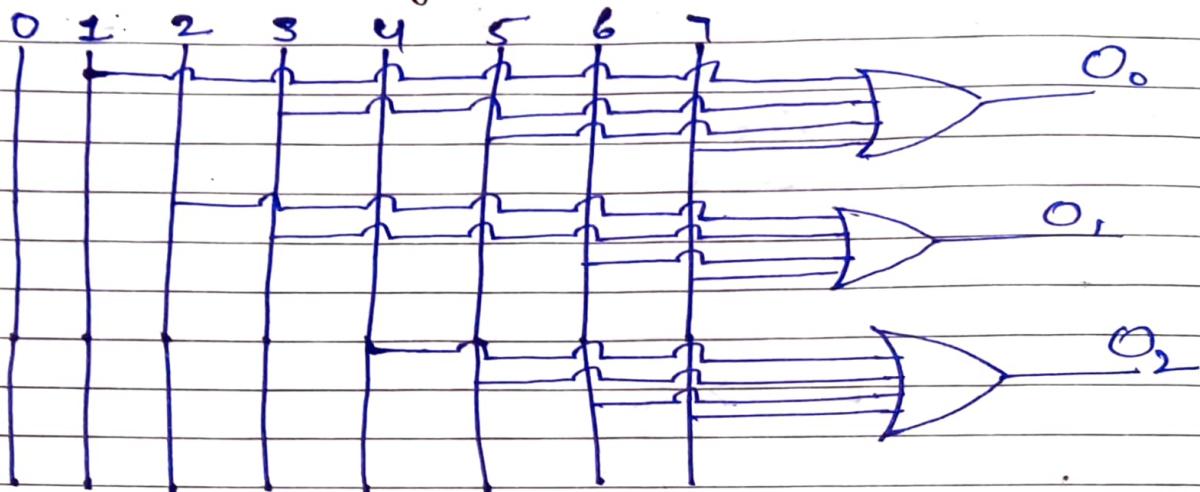

(+) Decimal to BCD Encoder :- 10; 4 line Encoder

10 - Input line


4 - output line

Input	Output								
D	D	C	B	A		1	3	Decimal	A
0	0	0	0	0		2	4	to	B
1	0	0	0	1		6	8	BCD	C
2	0	0	1	0		7	9	encoder	D
3	0	0	1	1					
4	0	1	0	0					
5	0	1	0	1					
6	0	1	1	0					
7	0	1	1	1					
8	1	0	0	0					
9	1	0	0	1					

Decimal to BCD encoder


$D \rightarrow 8 + 9$
 $C \rightarrow 4 + 5 + 6 + 7$
 $B \rightarrow 2 + 3 + 6 + 7$
 $A \rightarrow 1 + 3 + 5 + 7 + 9$

Decimal

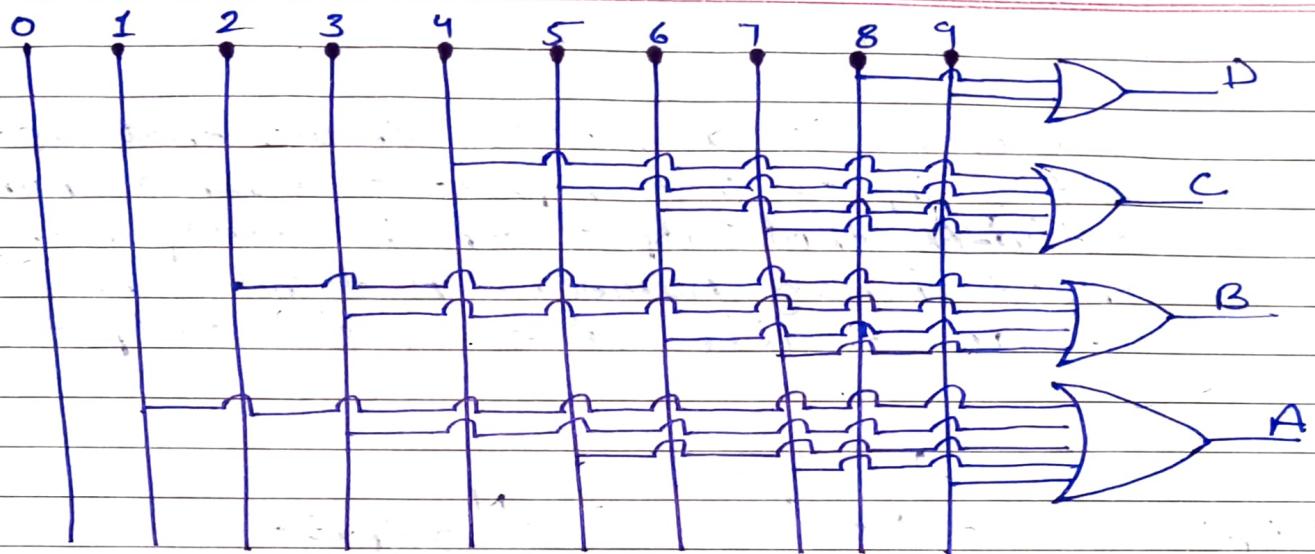

Decoder in digital Electronics:-

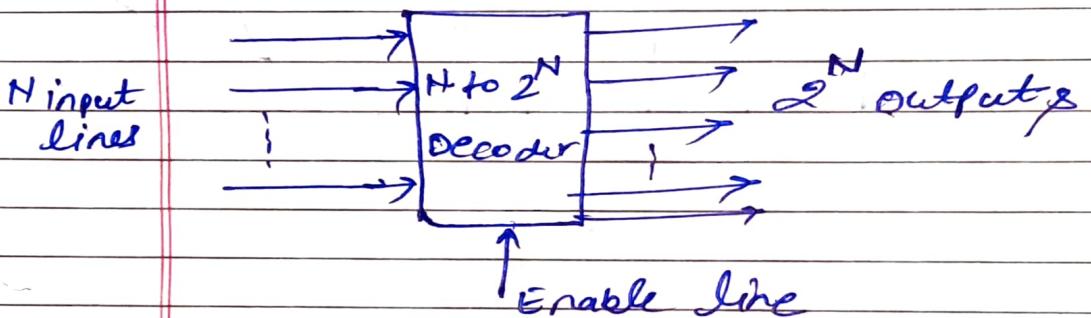A decoder is a logic circuit that accepts a set of inputs that represent a binary number & activates that output which corresponding to the input binary number. A decoder has 'n' inputs & an enable line & ' 2^n ' output lines.




④ 2 to 4 Decoder in Digital Electronics

It is a combinational circuit that converts the 2 bit binary information into 4 bit binary info. on basis of Enable signal.

Inputs :- A_0, A_1, E (enable line)

Outputs :- Y_0, Y_1, Y_2, Y_3

Block Diagram:-

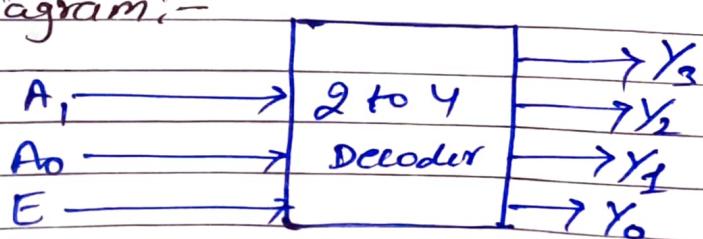

Truth Table :- when the Enable Signal (E) is 1,
One of the outputs is 1 & the rest
corresponds to 0. Here is

Enable	Input		Output			
E	A ₁	A ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


$$Y_3 = E, A_1 \cdot A_0$$

$$Y_2 = E A_1' A_0'$$

$$Y_1 = E A_1' A_0$$

$$Y_0 = E A_1 A_0'$$

Logic circuit :-

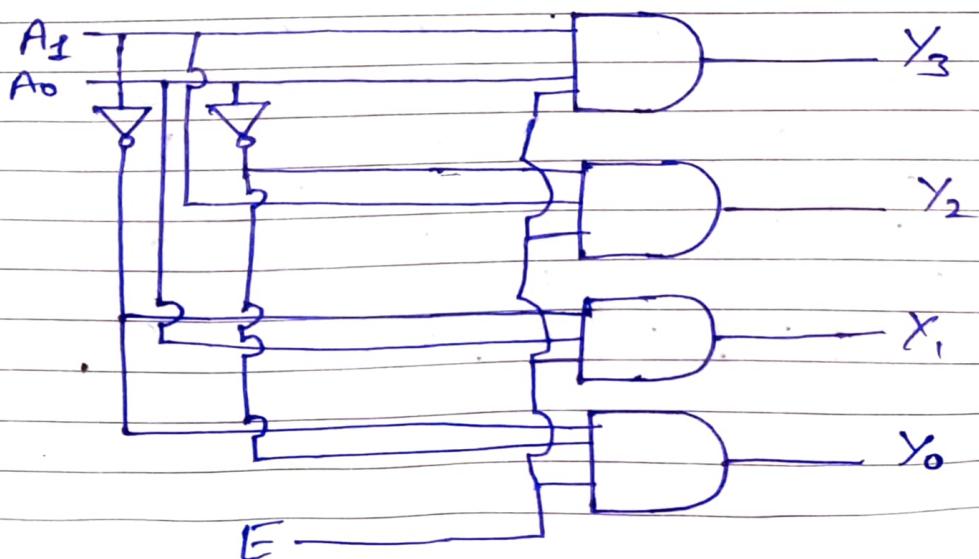


3 to 8 Decoder :- The 3 to 8 Decoder is responsible for converting 3-bit data to 8-bit data. It can be better understood by keeping in mind, that from 3 bits of data, maximum 8 numbers of combinations are possible.

Input:- A_0, A_1, A_2

Output:- $y_0, y_1, y_2, y_3, y_4, y_5, y_6, y_7$

Block Diagram :-

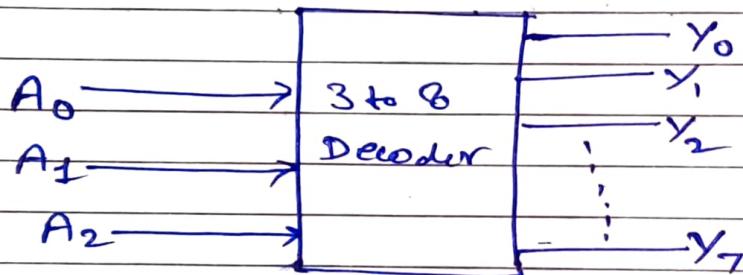

Truth Table

$$Y_0 = A'_0 \quad A'_1 \quad A'_2$$

$$Y_1 = A_0 \quad A'_1 \quad A'_2$$

$$Y_2 = A'_0 \quad A_1 \quad A'_2$$


$$Y_3 = A_0 \quad A_1 \quad A'_2$$

$$Y_4 = A'_0 \quad A'_1 \quad A_2$$

$$Y_5 = A_0 \quad A'_1 \quad A_2$$

$$Y_6 = A'_0 \quad A_1 \quad A_2$$

$$Y_7 = A_0 \quad A_1 \quad A_2$$

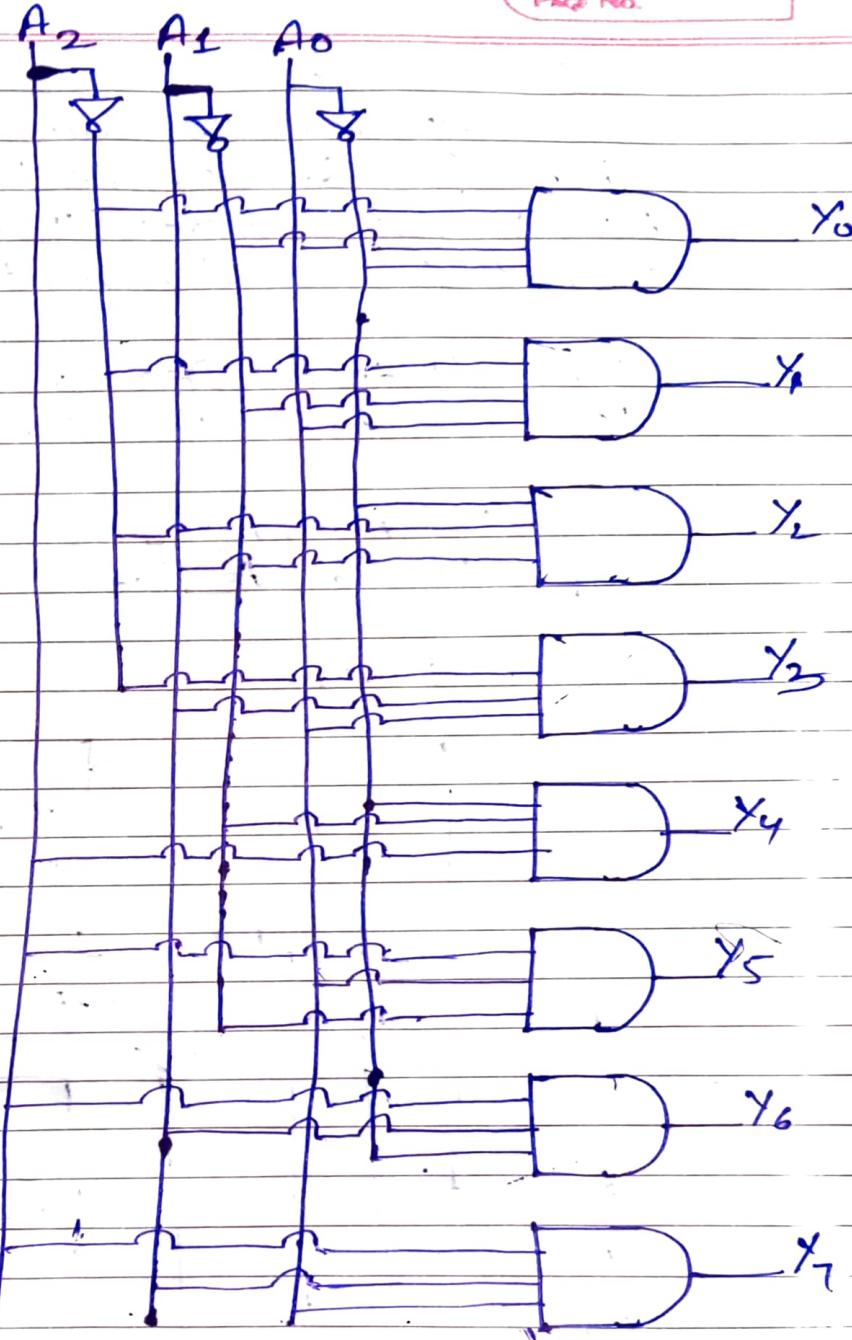


② 4 to 16 Decoder :- Now since the maximum number of combinations possible from 4 bits is 16. So, the 4 to 16 Decoder in digital Electronics converts 4-bit input data into 16-bit output binary information.

This 4 to 16 Decoder is constructed using two 3 to 8 Decoders.

Inputs:- A_0, A_1, A_2

outputs:- y_0 to y_{15}

Block Diagram:-

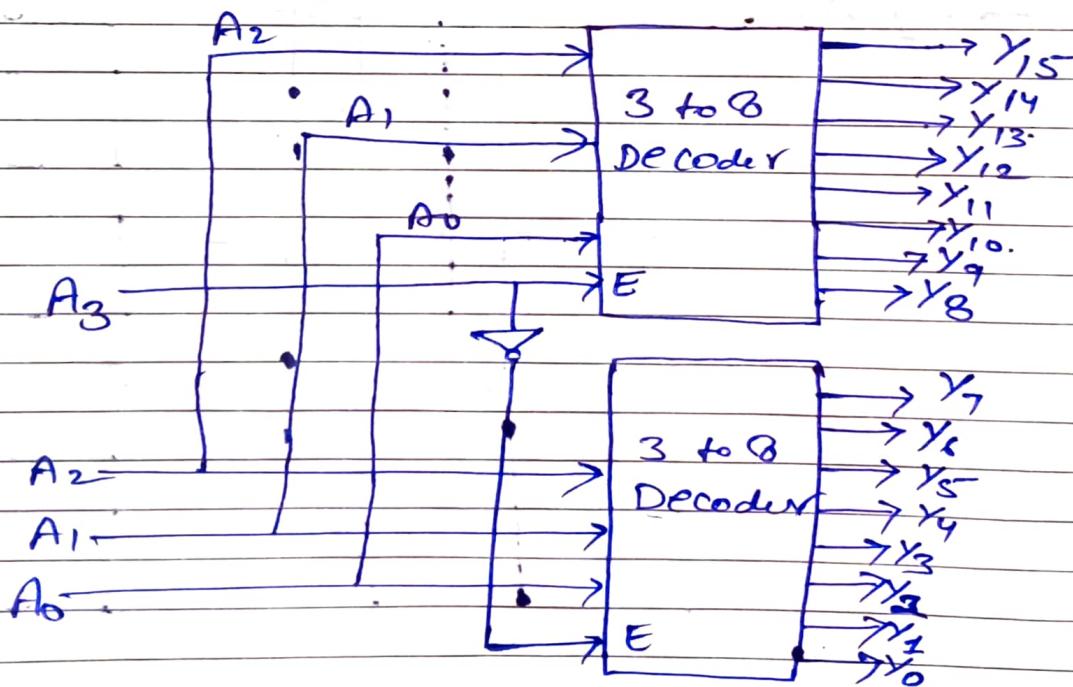

Inputs	A_3	A_2	A_1	A_0	Outputs
— — — —	—	—	—	—	Y_5
— — — —	—	—	—	—	Y_4
— — — —	—	—	—	—	Y_3
— — — —	—	—	—	—	Y_2
— — — —	—	—	—	—	Y_1
— — — —	—	—	—	—	Y_0
— — — —	—	—	—	—	Y_5
— — — —	—	—	—	—	Y_4
— — — —	—	—	—	—	Y_3
— — — —	—	—	—	—	Y_2
— — — —	—	—	—	—	Y_1
— — — —	—	—	—	—	Y_0
— — — —	—	—	—	—	Y_5
— — — —	—	—	—	—	Y_4
— — — —	—	—	—	—	Y_3
— — — —	—	—	—	—	Y_2
— — — —	—	—	—	—	Y_1
— — — —	—	—	—	—	Y_0

Multiplexer:- Multiplexer, also known as MUX, are essential components in digital electronics. Multiplexer in digital electronics is widely used for data selection, signal routing, & address decoding in microprocessors & microcontrollers. They are also used in communication systems to transmit multiple signals over a single channel.

Types:- (i) 2 to 1 multiplexer

(ii) 4 to 1 multiplexer

(iii) 8 to 1 multiplexer


(iv) 16 to 1 multiplexer

What is multiplexing:- It is the process of transmitting multiple signals or data streams over a single communication channel or transmission medium. This is achieved by combining multiple input signals into a single output signal and then transmitting it over a shared communication channel.

Multiplexer in Digital Electronics:- A multiplexer in digital electronics is known as a data selector. It is a combinational logic circuit having multiple input lines, one output line, & many select line or control lines. It receives binary information from several input lines & routes it to a single output line based on a set of select/control lines. Multiplexer in digital electronics is also known as many to one


combinational circuits.

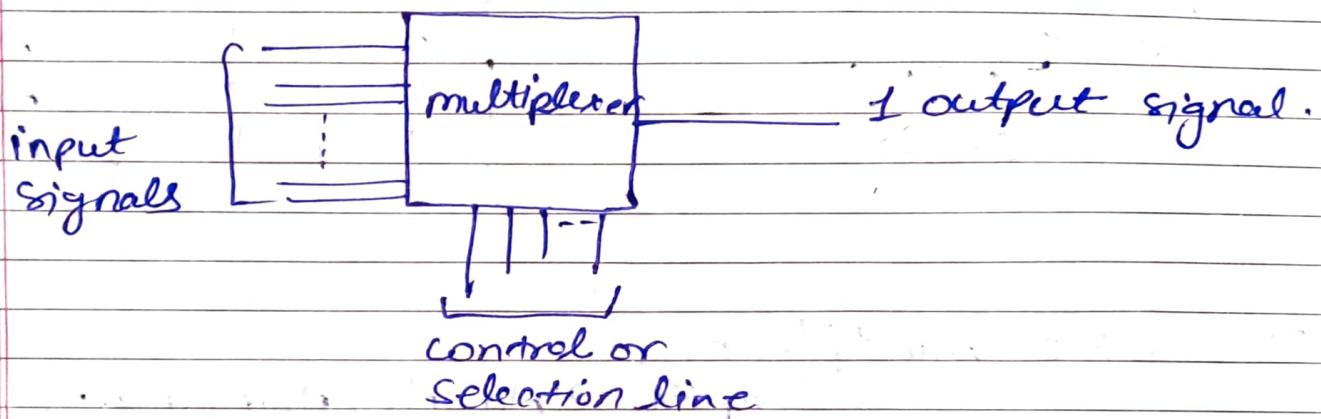The block diagram below depicts a multiplexer with n input lines, m selection lines, and one output line. If there are m selection/control lines, the number of possible input lines are 2^m .



Types:-

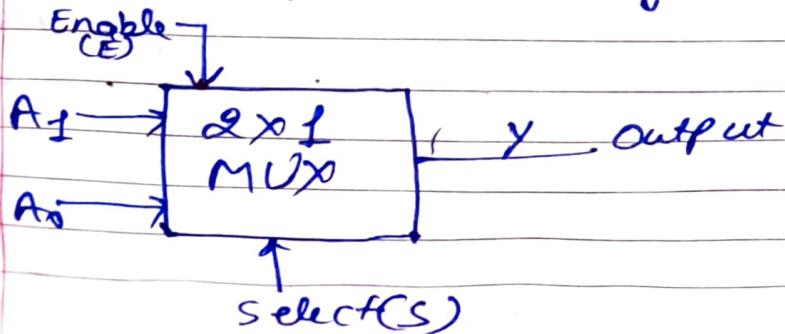(1) 2×1 multiplexer:- It is a combinational logic circuit that has only two inputs i.e. A_0 & A_1 , 1 selection line, i.e. S_0 & single output Y . On the basis of the combination of inputs that are present at the selection line S_0 , one of these 2 inputs forwards to the output line. It is the simplest type of multiplexer in digital electronics.




Truth Table:-

Inputs	Outputs
S_0 0	y A_0
1	A_1

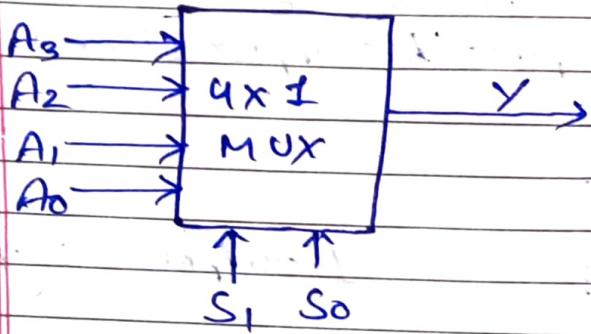(2)

4×1 multiplexer :-
 input $\rightarrow A_0, A_1, A_2, A_3$
 output $\rightarrow Y$
 selection line $\rightarrow S_1, S_0$




Inputs		Outputs	
S_1	S_0	S_0	Y
0	0	0	A_0
0	1	1	A_1
1	0	0	A_2
1	1	1	A_3

(3)

8×1 multiplexer :-

Inputs $\rightarrow A_0, A_1, A_2, A_3, A_4, A_5, A_6, A_7$
 Selection line $\rightarrow S_2, S_1, S_0$
 Output line $\rightarrow Y$

Enable (E)

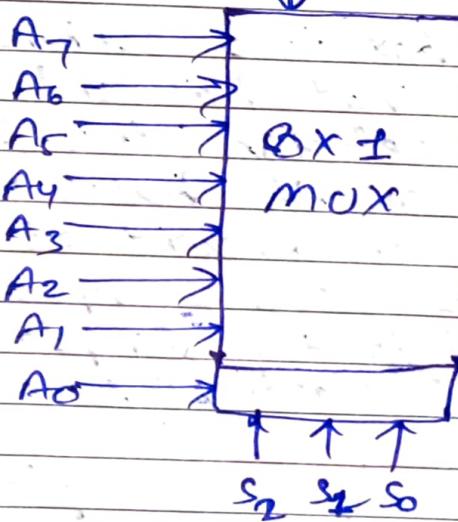

Inputs			Outputs	
S_2	S_1	S_0	S_0	Y
0	0	0	0	A_0
0	0	1	1	A_1
0	1	0	0	A_2
0	1	1	1	A_3
1	0	0	1	A_4
1	0	1	0	A_5
1	1	0	0	A_6
1	1	1	1	A_7